

CS61C: Great Ideas in Computer Architecture (aka Machine Structures)

Lecture 12: SDS Part 2

Instructors: Justin Yokota

Agenda

- Simplifying Circuits
 - Boolean Logic
- Finite State Machines


Agenda

- **Simplifying Circuits**
 - Boolean Logic
- Finite State Machines


Boolean Algebra

- Every function from $\{0,1\}^N \rightarrow \{0,1\}$ has a corresponding truth table
- Truth tables often have multiple circuits and logical expressions that compute their function
- Need standardized way to notate boolean expressions.
- Boolean Algebra: Use math notation to write basic logic operators (OR, AND, and NOT)


Boolean Algebra

 

AND: Notated as multiplication

 

OR: Notated as addition

 


NOT: Notated with overline

1 = TRUE, 0 = FALSE

Boolean Simplification Rules

AND Form	OR Form	
$x \cdot y = y \cdot x$	$x + y = y + x$	Commutativity
$(xy)z = x(yz)$	$(x + y) + z = x + (y + z)$	Associativity
$x \cdot 1 = x$	$x + 0 = x$	Identity
$x \cdot 0 = 0$	$x + 1 = 1$	Laws of 0's and 1's
$xy + x = x$	$(x + y)x = x$	Uniting Theorem
$x(y + z) = xy + xz$	$x + yz = (x + y)(x + z)$	Distributivity
$x \cdot x = x$	$x + x = x$	Idempotence
$x \cdot \bar{x} = 0$	$x + \bar{x} = 1$	Inverse (Complement)
$\overline{(xy)} = \bar{x} + \bar{y}$	$\overline{(x + y)} = \bar{x} \cdot \bar{y}$	DeMorgan's Laws

 Can we make an equivalent circuit with fewer gates?



Equivalent Boolean Expression:

$$((AB)+B)+C$$

$$= B+C$$

Simplifying Sum of Products

$\bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}C + AB\bar{C}$ (21 gates)

$\bar{A}\bar{B}C + \bar{A}B(\bar{C} + C) + A\bar{B}C + AB\bar{C}$

$\bar{A}\bar{B}C + \bar{A}B(1) + A\bar{B}C + AB\bar{C}$

$\bar{A}\bar{B}C + \bar{A}B + A\bar{B}C + AB\bar{C}$

$\bar{A}(\bar{B}C + B) + A\bar{B}C + AB\bar{C}$

$\bar{A}(\bar{B}C + B + BC) + A\bar{B}C + AB\bar{C}$

$\bar{A}(B + \bar{B}C + BC) + A\bar{B}C + AB\bar{C}$

$\bar{A}(B + (\bar{B} + B)C) + A\bar{B}C + AB\bar{C}$

$\bar{A}(B + C) + A\bar{B}C + AB\bar{C}$

$\bar{A}(B + C) + A(\bar{B}C + B\bar{C})$ (10 gates)

Can we do better? Yes (with different simplification order)

Best I could find: $(B + C)(!(ABC)) = 5$ gates

A	B	C	Out
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

Bad News

- Is it possible to algorithmically determine the fewest gates for a given Boolean Expression?
 - No known algorithm in polynomial time
 - If you do find one, $P = NP$
- Does a randomly generated circuit have a small circuit?
 - No; Sum of Products is asymptotically optimal in expectation

Good News

We're not dealing with random Boolean expressions!

- Mathematical operations have meaning behind them
 - Tends to lead to simple circuits
- The operations we mandate in RV32 base are precisely the ones with simple circuits
- RV32's instruction translations are chosen specifically to simplify the circuit

Often it's possible to find "patterns" in a truth table and get a small circuit that way

In most cases, we don't expect you to get the absolute smallest circuit for a given truth table

Simplify the truth table (Out0 and Out1 equations)

You may use XOR, represented by $\wedge$

But that uses however many gates
you used earlier to make XOR (OR,
AND, NOT count 1 each)

SOP score: 31 total gates


Gold Medal: 15 total gates

Platinum Medal: 12 gates

A	B	C	Out1	Out0
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1







Simplify the truth table (Out0 and Out1 equations)

 This circuit is known as a "full adder"
(Adds $A+B+C$)




A	B	CIn	COut	Out0
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

      Using AND, NOT, OR, and XOR, create a MUX gate



Sel	Out
0	In0
1	In1

 Create a 32-bit Adder using this subcircuit



SOP Score: ~32 sextillion
Gold Medal: 500 gates
Platinum Medal: 360 gates

A	B	Out0
0x00000000	0x00000000	0x00000000
0x00000000	0x00000001	0x00000001
0x00000000	0x00000002	0x00000002
0x00000000	0x00000003	0x00000003
...	...	...
0xDEADBEEF	0x12345678	0xF0E21567
...	...	...
0xFFFFFFFF	0xFFFFFFFF	0xFFFFFFFFE

Scratch Space

Agenda



- Simplifying Circuits
 - Boolean Logic
- **Finite State Machines**

Finite State Machines

- A simplified computing model
- Variations exist in other classes
 - CS 70 talks about probabilistic FSMs (Markov Chains)
 - CS 172 goes into DFAs and NDFAs
- If you know about FSMs from other classes, the variant we use in this class:
 - Receives one input per cycle
 - Outputs one value per cycle, instead of having a set of accepting states
 - Starting state, no stopping states



Finite State Machines

  - A Finite State Machine consists of a set of **states**





Finite State Machines

  - A Finite State Machine consists of a set of **states**
- Computation is done in **clock cycles**




Finite State Machines

  - A Finite State Machine consists of a set of **states**
- Computation is done in **clock cycles**
- Every clock cycle, the FSM receives an input




Finite State Machines

 - A Finite State Machine consists of a set of **states**
- Computation is done in **clock cycles**
- Every clock cycle, the FSM receives an input
 - Based on the input and its current state, it:




Finite State Machines

 - A Finite State Machine consists of a set of **states**
- Computation is done in **clock cycles**
- Every clock cycle, the FSM receives an input
 - Based on the input and its current state, it:
 - Moves to a new state (potentially its own)



Finite State Machines

 - A Finite State Machine consists of a set of **states**
- Computation is done in **clock cycles**
- Every clock cycle, the FSM receives an input
 - Based on the input and its current state, it:
 - Moves to a new state (potentially its own)
 - Outputs a value




Finite State Machines

Example: Say we start at state 0, and send this input:

0b0110110110111011100010110

What is the resulting output?

0b

 


Finite State Machines

Example: Say we start at state 0, and send this input:

0b0110110110111011100010110

What is the resulting output?

0b

 


Finite State Machines

Example: Say we start at state 0, and send this input:

0b0110110110111011100010110

What is the resulting output?

0b0

 


Finite State Machines

Example: Say we start at state 0, and send this input:

0b0**1**10110110111011100010110

What is the resulting output?

0b0

 


Finite State Machines

Example: Say we start at state 0, and send this input:

0b0**1**10110110111011100010110

What is the resulting output?

0b0**0**

 


Finite State Machines

Example: Say we start at state 0, and send this input:

0b0110110110111011100010110

What is the resulting output?

0b00

 


Finite State Machines

Example: Say we start at state 0, and send this input:

0b0110110110111011100010110

What is the resulting output?

0b001

 


Finite State Machines

Example: Say we start at state 0, and send this input:

0b011011011011100010110

What is the resulting output?

0b001

 


Finite State Machines

Example: Say we start at state 0, and send this input:

0b011011011011100010110

What is the resulting output?

0b0011

 


Finite State Machines

Example: Say we start at state 0, and send this input:

0b0110110110111011100010110

What is the resulting output?

0b0011011011011101110001011

 

Finite State Machines


Example: Say we start at state 0, and send this input:

0b0110110110111011100010110

What is the resulting output?

0b0011011011011101110001011

What does this FSM compute?

 

Finite State Machines

Example: Say we start at state 0, and send this input:


0b0110110110111011100010110

What is the resulting output?

0b0011011011011101110001011

What does this FSM compute?

 Outputs input from one cycle before (or input $\gg 1$)



Finite State Machines

Say we start at state 0, and send this:

0b0110110110111011100010110


What is the resulting output?

0b0011011011011101110001011


What does this FSM compute?

Outputs input from one cycle before

State	Input	Output	Next
0	0	0	0
0	1	0	1
1	0	1	0
1	1	1	1

 

What does this FSM do?

 

Draw a FSM

Draw a FSM that outputs 1 precisely when the most recent two bits are different.

Example:

Input: 01101101101101000010110

Output: 01011011011011100011101

Draw a FSM (Hard)

Draw a FSM that, when given the bitwise representation of N , outputs the bitwise representation of $N//5$

Example:

Input: 01101101101101000010110 = 3594774

Output: 00010101111100001101010 = 718954

Why are FSMs relevant?

- A RISC-V Processor is an FSM!
 - States?
 - N-tuple of registers and memory ($2^{32 \times 32 + \text{num bits in memory}}$ states)
 - Inputs?
 - 32-bit instruction (one per clock cycle)
 - FSMs can receive inputs that aren't just bits!
 - Outputs?
 - Print output, otherwise output ignored

Why are FSMs relevant?

- An FSM can be constructed using a circuit!
 - Main approach:
 - At start of clock cycle, send input (somehow)
 - Compute output and new state from input and current state (somehow)
 - Save new state in state elements (somehow)
 - Repeat every clock cycle
 - Combinational logic can be used to compute next state and next output given input and current state
 - Worst-case: Use SOP (though we can do way better)
 - Need a way to "save" what the current state is
 - Need a way to periodically start new clock cycles
 - Tomorrow!