

CS61C: Great Ideas in Computer Architecture (aka Machine Structures)

Lecture 14: Single-Cycle Datapath I

Instructor: Ariana Abel

Slides Credit: Justin Yokota

Ariana Abel

CS 61C

Summer 2025

- CS & Math Major
- Super Senior 😏
- 5th time teaching 61C
- I <3 computer hardware
- Interests: **C**rocheting, **C**offee, and **C**oncerts



Agenda

- Building a RISC-V Processor
- CPU Elements and Stages
- R-Type: add Datapath
- R-Type: sub Datapath
- Datapath with immediates: addi
- Implementing Loads
- Implementing Stores
- Implementing Jumps

Agenda

- **Building a RISC-V Processor**
- CPU Elements and Stages
- R-Type: add Datapath
- R-Type: sub Datapath
- Datapath with immediates: addi
- Implementing Loads
- Implementing Stores
- Implementing Jumps

Great Idea #1: Abstraction

(Levels of Representation/Interpretation)



High Level Language
Program (e.g., C)

Compiler

Assembly Language
Program (e.g., RISC-V)

Assembler

Machine Language Program
(RISC-V)

```
temp = v[k];  
v[k] = v[k+1];  
v[k+1] = temp;
```

```
lw    x3, 0(x10)  
lw    x4, 4(x10)  
sw    x4, 0(x10)  
sw    x3, 4(x10)
```


```
1000 1101 1110 0010 0000 0000 0000 0000  
1000 1110 0001 0000 0000 0000 0000 0100  
1010 1110 0001 0010 0000 0000 0000 0000  
1010 1101 1110 0010 0000 0000 0000 0100
```

Hardware Architecture Description
(e.g., block diagrams)

Architecture Implementation

Logic Circuit Description
(Circuit Schematic Diagrams)

Old-school Machine Structures

 

New-school Machine Structures

Software

Parallel Requests

Assigned to computer
e.g., Search “Cats”

Parallel Threads

Assigned to core e.g., Lookup, Ads

Parallel Instructions

>1 instruction @ one time
e.g., 5 pipelined instructions

Parallel Data

>1 data item @ one time
e.g., Add of 4 pairs of words

Hardware descriptions

All gates work in parallel at same time


Harness Parallelism &
Achieve High Performance

Hardware

Warehouse
Scale
Computer




Smart
Phone

 

How do we build a Single-Core Processor?

Processor (CPU):
the active part of
the computer that
does all the work
(data manipulation
and decision-
making).


- Ultimately just a complicated circuit

 

How do we build a Single-Core Processor?

Datapath (“the brawn”):
portion of the processor that contains hardware necessary to perform operations required by the processor.

 Control (“the brain”):
portion of the processor (also in hardware) that tells the datapath what needs to be done.



Goal: Design HW to Execute All RV32I Instructions

CS Open  Reference Card

Base Integer Instructions: RV32I

Category	Name	Fmt	RV32I Base	Category	Name	Fmt	RV32I Base
Shifts	Shift Left			Loads	Load		
Logical		R	SLL rd,rs1,rs2	Byte		I	LB rd,rs1,imm
	Shift Left Log. Imm.	I	SLLI rd,rs1,shamt		Load Halfword	I	LH rd,rs1,imm
	Shift Right Logical	R	SRL rd,rs1,rs2		Load Byte Unsigned	I	LBU rd,rs1,imm
	Shift Right Log. Imm.	I	SRLI rd,rs1,shamt		Load Half Unsigned	I	LHU rd,rs1,imm
	Shift Right Arithmetic	R	SRA rd,rs1,rs2		Load Word	I	LW rd,rs1,imm
	Shift Right Arith. Imm.	I	SRAI rd,rs1,shamt	Stores	Store		
Arithmetic				Byte		S	SB rs1,rs2,imm
ADD		R	ADD rd,rs1,rs2		Store Halfword	S	SH rs1,rs2,imm
	ADD Immediate	I	ADDI rd,rs1,imm		Store Word	S	SW rs1,rs2,imm
	SUBtract	R	SUB rd,rs1,rs2	Branches			
	Load Upper Imm	U	LUI rd,imm	Branch =		B	BEQ rs1,rs2,imm
	Add Upper Imm to PC	U	AUIPC rd,imm	Branch <		B	BLT rs1,rs2,imm
Logical				Branch >=		B	BGE rs1,rs2,imm
XOR		R	XOR rd,rs1,rs2	Branch < Unsigned		B	BLTU rs1,rs2,imm
	XOR Immediate	I	XORI rd,rs1,imm	Branch >= Unsigned		B	BGEU rs1,rs2,imm
	OR	R	OR rd,rs1,rs2	Jump & Link			
	OR Immediate	I	ORI rd,rs1,imm	J&L		J	JAL rd,imm
	AND	R	AND rd,rs1,rs2	Jump & Link Register		I	JALR rd,rs1,imm
	AND Immediate	I	ANDI rd,rs1,imm				
Compare				Synch	Synch	I	FENCE
Set <		R	SLT rd,rs1,rs2	thread			
	Set < Immediate	I	SLTI rd,rs1,imm				
	Set < Unsigned	R	SLTU rd,rs1,rs2	Environment			
	Set < Imm Unsigned	I	SLTIU rd,rs1,imm	CALL		I	ECALL
				BREAK		I	EBREAK

Summer 2025



HiFive Unmatched (RISC-V Linux)


<https://www.sifive.com/boards/hifive-unmatched>

Agenda

- Building a RISC-V Processor
- **CPU Elements and Stages**
- R-Type: add Datapath
- R-Type: sub Datapath
- Datapath with immediates: addi
- Implementing Loads
- Implementing Stores
- Implementing Jumps

One-Instruction-Per-Cycle RISC V Machine

 The CPU is composed of two types of subcircuits: **combinational logic blocks** and **state elements**.



One-Instruction-Per-Cycle RISC V Machine

- On **every tick of the clock**, the computer executes one instruction:
 - Current outputs of the state elements drive the inputs to combinational logic
- At the **rising clock edge**:
 - All the state elements are updated with the combinational logic outputs...
 - and execution moves to the next clock cycle.
- The **state elements** determine the behavior of the CPU

Combinational Logic Blocks

- Any function can be built using **AND, OR, and NOT** gates.
- Examples:
 - Adder
 - Multiplexer (MUX): selects one input based on a selector.
- Wires carry 0 or 1 (low vs high voltage).
- All logic runs simultaneously (not controlled by clock)
- Each logic block has a **delay**
 - how long it takes for that block to compute its function

State Elements

- State elements store the current *data* of the program
- RISC-V is designed to work according to state elements ONLY
 - E.g. If two CPUs have the exact same values in all state elements, then both CPUs will perform the exact same sequence of operations. What the CPU does is determined *solely* by a current snapshot of all state elements.
- Every instruction modifies some state elements (otherwise the program would infinite-loop)
- Three main state elements in the CPU:
 - Registers (PC)
 - RegFile
 - Main Memory

State Element: Register

Input:


- 32-bit data input bus (D)
- Write Enable “Control” bit (1 = Enabled, 0 = Disabled)

Output:

- 32-bit data output bus (Q)

Behavior:

 
- If Write Enable is 1 on rising clock edge, set Data Out=Data In.
- At **all other times**, Data Out will not change; it will output its current value.
- Note: **Reading** the value of a register doesn't take a clock tick. Only **Writing** to the register takes a tick.



State Element: Register File

Group of 32 registers; manages which registers get changed and which register outputs get read

 
- Input:
 - One 32-bit input bus, *dataW*.
 - Three 5-bit selectors, *rs1*, *rs2*, and *rsW*.
 - RegWEn control bit (Write Enabled).
- Output:
 - Two 32-bit output busses, *data1* and *data2* (The data in *rs1* and *rs2*).



State Element: Register File

Registers are accessed via their 5-bit register numbers:

 
- rs1: 5-bit number that identifies which register should output in data1
- rs2: 5-bit number that identifies which register should output in data2
- rsW: 5-bit number that identifies which register should update next cycle



State Element: Register File

Clock behavior:

 
- If **RegWEn** is 1 on rising clock edge, set $rsW = DataW$.
- **Reading** the value of a register doesn't take a clock tick. Only **Writing** to the register takes a tick.



State Element: Memory

Main memory: Allows access to each byte saved in the program

 
- Input:
 - One 32-bit input bus, *addr*.
 - One 32-bit input bus, *dataW*
 - MemRW control bit (Write Enabled).
- Output:
 - One 32-bit output bus, *dataR* (The word stored at *addr*).



State Element: Memory


For now, main memory is "magic".

 - Acts *similar* to the Regfile (ex. put in an address, get out the data at that address).
 - Clock behaves the same way
- But registers are too expensive, so some other underlying technology gets used.



State Element: IMEM vs DMEM

- Current abstraction: Memory holds both instructions and data in one contiguous 32-bit memory space.
- In our processor, we'll use two "separate" memories:
 - **IMEM**: A *read-only* memory for fetching instructions.
 - **DMEM**: A memory for loading (read) and storing (write) data words.
 - Under the hood, these are placeholders for caches.
- Because IMEM is read-only, it never requires a clock trigger, dataW, etc.

 


Designing the Datapath

All instructions follow the same general 5 "stages" of computation


Designing the Datapath

 "Instruction Fetch" (IF): Send PC into IMEM, retrieve the instruction to be run.




Designing the Datapath

 "Instruction Decode" (ID): Read instruction, decode what the instruction is meant to do, compute immediates/register values.




Designing the Datapath

 "Execute" (EX): Do any computations needed for the instruction.




Designing the Datapath

 "Memory" (MEM): For DMEM operations, a separate stage for accessing memory.



Designing the Datapath

 "Write Back" (WB): Update inputs to any state elements that need to be updated, wait for next rising edge to actually write data back



Designing the Datapath

All instructions follow the same general "stages" of computation:

- "Instruction Fetch" (IF): Send PC into IMEM, retrieve the instruction to be run.
- "Instruction Decode" (ID): Read instruction, decode what the instruction is meant to do, compute immediates/register values.
- "Execute" (EX): Do any computations needed for the instruction.
 - "Memory" (MEM): For DMEM operations, a separate stage for accessing memory.
- "Write Back" (WB): Update inputs to any state elements that need to be updated, wait for next rising edge to actually write data back


For a single-stage datapath, all stages happen in **a single clock cycle**.

Datapath Design Philosophy

- Every logic block/state element in a CPU needs to do something each cycle, but all blocks run simultaneously.
- General philosophy: do **every single operation** for every instruction, even if the result doesn't make sense. But add **control logic** to ensure that only the operations we *want* end up affecting state elements.

Datapath Design Philosophy

- Important tool here is the **multiplexer (mux)**: Receive multiple inputs (ex. $a+b$, $a-b$, $a|b$) and a selector (ex. "I want the ADD result"), and output the corresponding input ($a+b$).

 

Datapath Design Philosophy

- For the rest of this lecture and Thursday's: Building the datapath, one instruction at a time.

Agenda

- Building a RISC-V Processor
- CPU Elements and Stages
- **R-Type: add Datapath**
- R-Type: sub Datapath
- Datapath with immediates: addi
- Implementing Loads
- Implementing Stores
- Implementing Jumps


Implementing the add instruction

- For now, let's imagine that the only instruction we have is "add"
- Since add doesn't use memory, we will not use a DMEM yet. But all other parts of the datapath are needed.
- add does two things to state elements:
 - Sets rd to $rs1 + rs2$
 - Sets PC to $PC + 4$


Instruction	Name	Description	Type	Opcode	Funct3	Funct7
add rd rs1 rs2	ADD	rd = rs1 + rs2	R	011 0011	000	000 0000

31	25	24	20	19	15	14	12	11	7	6	0
R	funct7		rs2		rs1		funct3		rd		opcode

 Implementing add (example: add x5 x6 x7): IF




 Implementing add (example: add x5 x6 x7): ID




Note: rs1 always inst[19:15], rs2 always inst[24:20], rd always inst[11:7] if they exist

 Implementing add (example: add x5 x6 x7): EX



 Implementing add (example: add x5 x6 x7): WB



Agenda


- Building a RISC-V Processor
- CPU Elements and Stages
- R-Type: add Datapath
- **R-Type: sub Datapath**
- Datapath with immediates: addi
- Implementing Loads
- Implementing Stores
- Implementing Jumps

Implementing the sub instruction


- Let's add another R-type instruction: sub
- sub does two things to state elements:
 - Sets rd to rs1-rs2
 - Sets PC to PC+4
- Main idea: Do both addition and subtraction, and use a mux to decide which one to output

Instruction	Name	Description	Type	Opcode	Funct3	Funct7
add rd rs1 rs2	ADD	rd = rs1 + rs2	R	011 0011	000	000 0000
sub rd rs1 rs2	SUBtract	rd = rs1 - rs2	R	011 0011	000	010 0000

 
add Datapath: What do you need to add to handle sub?




add/sub Datapath

 

add/sub Datapath running add x5 x6 x7

 

add/sub Datapath running sub x5 x6 x7

 


Deciding mux selectors

- How do we decide what selector to set for the mux?
 - Use the differences in opcode, funct3, or funct7
- In this case: Bit 6 of the funct7 is 1 for sub, 0 for add. So we can send bit 30 of the instruction (which is bit 6 of funct7) to the mux selector
- For more complicated cases: We'll abstract it away for now in a combinational logic block we'll call the **control logic**
 - Control logic takes in the instruction, and outputs all mux selectors and WENs needed for the instruction


Instruction		Name	Description	Type	Opcode	Funct3	Funct7
add	rd rs1 rs2	ADD	$rd = rs1 + rs2$	R	011 0011	000	000 0000
sub	rd rs1 rs2	SUBtract	$rd = rs1 - rs2$	R	011 0011	000	010 0000

add/sub Datapath

 



Analogy: A king and his advisors

 - The datapath is a group of advisors: they do math according to their specialization and report their results
- The control logic is the king: they decide which advisor to listen to, based on what the kingdom needs.




Analogy: A king and his advisors

  - The datapath is a group of advisors: they do math according to their specialization and report their results
- The control logic is the king: they decide which advisor to listen to, based on what the kingdom needs.



Supporting all R-Type Instructions

 - Create a subcircuit called "ALU" (Arithmetic Logic Unit) to handle all math. Control logic decides which operation the ALU does.



Instruction		Name	Description	Type	Opcode	Funct3	Funct7
add	rd rs1 rs2	ADD	$rd = rs1 + rs2$	R	011 0011	000	000 0000
sub	rd rs1 rs2	SUBtract	$rd = rs1 - rs2$	R	011 0011	000	010 0000
and	rd rs1 rs2	bitwise AND	$rd = rs1 \& rs2$	R	011 0011	111	000 0000
or	rd rs1 rs2	bitwise OR	$rd = rs1 rs2$	R	011 0011	110	000 0000
xor	rd rs1 rs2	bitwise XOR	$rd = rs1 \wedge rs2$	R	011 0011	100	000 0000
sll	rd rs1 rs2	Shift Left Logical	$rd = rs1 \ll rs2$	R	011 0011	001	000 0000
srl	rd rs1 rs2	Shift Right Logical	$rd = rs1 \gg rs2$ (Zero-extend)	R	011 0011	101	000 0000
sra	rd rs1 rs2	Shift Right Arithmetic	$rd = rs1 \gg rs2$ (Sign-extend)	R	011 0011	101	010 0000
slt	rd rs1 rs2	Set Less Than (signed)	$rd = (rs1 < rs2) ? 1 : 0$	R	011 0011	010	000 0000
sltu	rd rs1 rs2	Set Less Than (Unsigned)		R	011 0011	011	000 0000

Agenda

- Building a RISC-V Processor
- CPU Elements and Stages
- R-Type: add Datapath
- R-Type: sub Datapath
- **Datapath with immediates: addi**
- Implementing Loads
- Implementing Stores
- Implementing Jumps


Implementing the addi instruction

- Let's add an I-type instruction: addi
- addi does two things to state elements:
 - Sets rd to rs1+imm
 - Sets PC to PC+4
- Same as add, but now we need a subcircuit to construct the immediate


addi	rd	rs1	imm	ADD Immediate	rd = rs1 + imm	I	001	0011	000	
------	----	-----	-----	---------------	----------------	---	-----	------	-----	--

I	imm[11:0]	rs1	funct3	rd	opcode
---	-----------	-----	--------	----	--------


R-Type Datapath

 


Datapath with addi

 


Datapath with addi

 

Datapath with addi: Running add x5 x6 x7

 

 
Datapath with addi: Running addi x5 x6 39



ImmGen design


- Need to convert imm to a full 32-bit value (to send to ALU)

 31 30 29 28 27 26 25 24 23 22 21 20 19 18 17 16 15 14 13 12 11 10 09 08 07 06 05 04 03 02 01 00




ImmGen design

 - Need to convert imm to a full 32-bit value (to send to ALU)
- Copy the bottom 12 bits of imm to the bottom 12 bits of output
- Then *sign-extend* by copying bit 11 to all remaining bits of output
- In ALL instruction formats, bit 31 is the sign bit of the immediate (except R-types, which don't have an immediate)



Datapath so far

 

Agenda


- Building a RISC-V Processor
- CPU Elements and Stages
- R-Type: add Datapath
- R-Type: sub Datapath
- Datapath with immediates: addi
- **Implementing Loads**
- Implementing Stores
- Implementing Jumps

Implementing the `lw` instruction


- Let's add `lw`
- `lw` computes one thing:
 - $\text{addr} = \text{rs1} + \text{imm}$
 - Adding $\text{rs1} + \text{imm}$ can be done using ALU in current datapath
- And affects two state elements:
 - $\text{rd} = \text{data at addr (4 bytes)}$
 - $\text{PC} = \text{PC} + 4$
- Requires adding DMEM *after* ALU, but *before* writing back to register

<code>lw</code>	<code>rd imm(rs1)</code>	Load Word	<code>rd = 4 bytes of memory starting at address <code>rs1 + imm</code></code>	I	000 0011	010	
-----------------	--------------------------	-----------	--	---	----------	-----	--

 
Datapath running lw x8 24(x2): IF, ID, EX



 Datapath running lw x8 24(x2): IF, ID, EX, MEM




Datapath running lw x8 24(x2)

 

DMEM Limitations

 - To simplify its circuitry, DMEM can ONLY access 32 bits at a time
- Also many RISC-V DMEMs can only access addresses that **are a multiple of 4**.
 - Ex. If you want data at 0xFFFF FFFF, you can access address 0xFFFF FFFC, but not 0xFFFF FFFD



DMEM Limitations Affect Programming

- Because of this inherent limitation, RISC-V often mandates that loads/stores happen on *aligned* addresses:
 - `lw/sw`: addr is multiple of 4
 - ex. `lw s0 3(sp)` is illegal unless `sp` is 1 mod 4
 - `lh/sh/lhu`: multiple of 2
 - `lb/sb/lbu`: can be run on any address
 - Other accesses yield undefined behavior: **the CPU can do anything if someone tries an unaligned access**

DMEM Limitations Affect Programming

- It's *possible* to create an unaligned access (pseudoinstruction-style) using only aligned accesses, but it's **much** slower.
 - Venus lets you use unaligned accesses despite this
 - Even in x86, which allows unaligned accesses, they take much longer to run
- This is why structs tend to place their components in a way that they're word-aligned, even if that wastes some space

DMEM Limitations Affect our Circuit: Loads

General procedure to handle loads:

1. Send into the DMEM the address of the word **containing your desired data**
 - a. Since only aligned accesses are allowed, no load will ever require data from two different 4-byte blocks
 - b. Ex. The byte starting at 0xDEADBEEF is contained with the 4-byte word starting at 0xDEADBEEC
2. Split the retrieved word into bytes/halfwords
3. Select the appropriate byte/halfword using $\text{address} \% 4$ and mux
4. Sign- or Zero-extend the resulting data to a full 32 bits

Exact implementation is an exercise in Project 3, and will be omitted for this lecture

Agenda


- Building a RISC-V Processor
- CPU Elements and Stages
- R-Type: add Datapath
- R-Type: sub Datapath
- Datapath with immediates: addi
- Implementing Loads
- **Implementing Stores**
- Implementing Jumps

Implementing the sw instruction


- Let's add sw
- sw computes one thing:
 - $\text{addr} = \text{rs1} + \text{imm}$
 - Note that this is the same as for lw. So we don't need to change our DMEM input.
- And affects two state elements:
 - $\text{DMEM}[\text{addr}] = \text{rs2}$
 - $\text{PC} = \text{PC} + 4$
- Main issues:
 - imm is now split into two parts
 - DMEM write, no RegFile write

sw	rs2 imm(rs1)	Store Word	Stores rs2 starting at the address rs1 + imm in memory		S	010 0011	010	
S	imm[11:5]	rs2	rs1	funct3	imm[4:0]	opcode		


Datapath so far

 

 
Datapath running sw s0 24(sp): Handling new imm type



 
Datapath running `sw s0 24(sp)`: Sending data to DMEM



 What values do you set for RegWEn, BSel, WBSel, WBSel?



 Datapath running sw s0 24(sp): Write Back



DMEM Limitations Affect our Circuit: Stores

As with loads, DMEM's limitations affect our circuit design.

General approach:

- Determine which word contains the data we will store
 - As with loads, no store to two separate words
- Manipulate the data to align with the right bytes
 - Left-shifts according to the endianness
- Use separate read/write bits for each byte, so you don't overwrite unnecessary data

Exact implementation is an exercise in Project 3, and will be omitted for this lecture

Agenda


- Building a RISC-V Processor
- CPU Elements and Stages
- R-Type: add Datapath
- R-Type: sub Datapath
- Datapath with immediates: addi
- Implementing Loads
- Implementing Stores
- **Implementing Jumps**

Implementing the jal instruction


- Let's add jal
- jal computes one thing:
 - New PC = PC + offset
 - Goal: Make the ALU do this math
- And affects two state elements:
 - rd = PC+4
 - PC = PC+offset
- Main issues:
 - ImmGen needs to handle J-type immediates (including adding the implicit 0)
 - WB to RegFile needs to include PC+4
 - WB to PC needs to include PC+offset
 - Send PC into ALU so it can compute PC+offset

jal	rd label	Jump And Link	rd = PC + 4 PC = PC + offset	J	110 1111	
J	imm[20 10:1 11 19:12]			rd	opcode	

 
Datapath so far: how do you handle J-Types?



 
Datapath running jal x1 100: Add ImmSel for J



 
Datapath running `jal x1 100`: Computing PC+offset in ALU



 
Datapath running jal x1 100: Setting PC to PC+Offset



 Datapath running jal x1 100: Setting rd to PC+4



Datapath running jalr x1 x5 100

 

Datapath so far

