

CS61C: Great Ideas in Computer Architecture (aka Machine Structures)

Lecture 15: Single-Cycle Datapath II

Instructor: Ariana Abel

Slides Credit: Justin Yokota


Agenda

- Implementing Branches
- Implementing U-types
- Implementing ImmGen
- Datapath and Control
 - Control Logic Design: ROM
 - Control Logic Design: Combinational Logic
- Instruction Timing

Agenda

- **Implementing Branches**
- Implementing U-types
- Implementing ImmGen
- Datapath and Control
 - Control Logic Design: ROM
 - Control Logic Design: Combinational Logic
- Instruction Timing

Datapath so far: R, I, S, J types

 

Implementing branch instructions


- Let's add beq
- beq compares rs1 and rs2:
 - Need new component for comparisons
- Then computes one thing:
 - New PC if branch = PC+offset
 - This uses the ALU, so can't use ALU for comparisons - need new block!
- Then sets one state element:
 - PC+4 if branch not taken, PC+offset if branch is taken
 - Can use PCSel
- Main issues:
 - Control logic (PCSel) needs to be conditioned on Branch result
 - New immediate type
 - New Branch Comparator

beq	rs1	rs2	label	Branch if Equal	if (rs1 == rs2) PC = PC + offset	B	110 0011	000
B	imm[12 10:5]	rs2	rs1	funct3	imm[4:1 11]	opcode		

Datapath so far

CS 61C


Summer 2025

 

Datapath running beq x5 x6 16

CS 61C

Summer 2025

 

The Branch Comparator


The Branch Comparator will handle all our branch instructions:

Input:


- Two data busses A and B (corresponding to rs1 and rs2)
- BrUn control bit: Do unsigned comparison?
 - Only affects BrLt, since == is the same regardless of signed vs unsigned

Output:

 - Two bits:
 - BrEq that's 1 if $A == B$
 - BrLt that's 1 if $A < B$
 - Note: $A \geq B$ is the same as $!(A < B)$, so no need for BrGe
- Can decide PCSel based on these outputs, so send to Control Logic



 Datapath running beq x5 x6 16 (equality holds)



CS 61C Summer 2025




Agenda

- Implementing Branches
- **Implementing U-types**
- Implementing ImmGen
- Datapath and Control
 - Control Logic Design: ROM
 - Control Logic Design: Combinational Logic
- Instruction Timing

Implementing lui

- Let's add lui
- lui computes a new immediate type
- And affects two state elements:
 - $rd = imm$
 - $PC = PC + 4$


<code>auipc rd immu</code>	Add Upper Immediate to PC	$imm = immu \ll 12$ $rd = PC + imm$	U	001 0111	
<code>lui rd immu</code>	Load Upper Immediate	$imm = immu \ll 12$ $rd = imm$	U	011 0111	

 


Implementing auipc

- auipc does the same thing as lui, but it also adds PC to the immediate value

<code>auipc rd immu</code>	Add Upper Immediate to PC	<code>imm = immu << 12</code> <code>rd = PC + imm</code>	U	001 0111	
<code>lui rd immu</code>	Load Upper Immediate	<code>imm = immu << 12</code> <code>rd = imm</code>	U	011 0111	

 


Datapath So Far

 

Datapath running lui x5 0x12345

CS 61C


Summer 2025

 


Datapath running auipc x5 0x12345

CS 61C

Summer 2025

 

Complete RISC-V Datapath!!!

 

Agenda

- Implementing Branches
- Implementing U-types
- **Implementing ImmGen**
- Datapath and Control
 - Control Logic Design: ROM
 - Control Logic Design: Combinational Logic
- Instruction Timing

What's Left?

With the datapath we have, we've reduced the problem of making a CPU to a few small subcircuits:

- **Multiplexers**: Discussed in previous lecture, and part of Lab 5
- **ALU/Regfile**: Implemented as part of Project 3A
- **Branch Comparator**: Implemented as part of Project 3B
- **IMEM/DMEM**: Exact implementation out of scope
- **Control Logic**: The big one
 - Later in lecture
- **ImmGen**: Let's finish this off right now
 - At the same time, we'll notice some clever patterns in how the bits are stored across instruction formats

How to make the ImmGen

Option 1:

- Make a circuit for each instruction format, then mux the results with ImmSel
- Ugly, but it works

Option 2:

- Look for patterns in the instruction format
- Takes time, but gives much greater insight into why instruction formats were designed this way

Instruction Formats

	31	25	24	20	19	15	14	12	11	7	6	0
R	funct7		rs2		rs1		funct3		rd		opcode	
I	imm[11:0]				rs1		funct3		rd		opcode	
I*	funct7		imm[4:0]		rs1		funct3		rd		opcode	
S	imm[11:5]		rs2		rs1		funct3		imm[4:0]		opcode	
B	imm[12 10:5]		rs2		rs1		funct3		imm[4:1 11]		opcode	
U	imm[31:12]								rd		opcode	
J	imm[20 10:1 11 19:12]								rd		opcode	

Tracking all Immediate Bits in each format

CS 61C

Summer 2025

Imm	31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
-----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	---	---	---	---	---	---	---	---	---	---

I	11	10	9	8	7	6	5	4	3	2	1	0																					
S	11	10	9	8	7	6	5														4	3	2	1	0								
B	12	10	9	8	7	6	5														4	3	2	1	11								
U	31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12													
J	20	10	9	8	7	6	5	4	3	2	1	11	19	18	17	16	15	14	13	12													

Tracking all Immediate Bits in each format

Imm	31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
-----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	---	---	---	---	---	---	---	---	---	---

Bit 0 of imm: Bit 20 of inst if I type, Bit 7 of inst if S type, always 0 if B/U/J type

I	11	10	9	8	7	6	5	4	3	2	1	0																				
S	11	10	9	8	7	6	5															4	3	2	1	0						
B	12	10	9	8	7	6	5															4	3	2	1	1	1					
U	31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12												
J	20	10	9	8	7	6	5	4	3	2	1	1	1	19	18	17	16	15	14	13	12											

Tracking all Immediate Bits in each format

Imm	31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
-----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	---	---	---	---	---	---	---	---	---	---

Bits 4-1 of imm: Bits 24-21 of inst if I/J type, Bits 11-8 of inst if S/B type, always 0 if U type. **Only found in two parts of the instruction, and these 4 bits are always together.**

I	11	10	9	8	7	6	5	4	3	2	1	0																				
S	11	10	9	8	7	6	5														4	3	2	1	0							
B	12	10	9	8	7	6	5														4	3	2	1	11							
U	31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12												
J	20	10	9	8	7	6	5	4	3	2	1	11	19	18	17	16	15	14	13	12												

Tracking all Immediate Bits in each format

Imm	31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
-----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	---	---	---	---	---	---	---	---	---	---

Bits 10-5 of imm: Bits 30-25 of inst if I/S/B/J type, always 0 if U type. **Only found in one part of the instruction, even though 4 different instruction formats use it!**

I	11	10	9	8	7	6	5	4	3	2	1	0																				
S	11	10	9	8	7	6	5															4	3	2	1	0						
B	12	10	9	8	7	6	5															4	3	2	1	11						
U	31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12												
J	20	10	9	8	7	6	5	4	3	2	1	11	19	18	17	16	15	14	13	12												

Tracking all Immediate Bits in each format

Imm	31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
-----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	---	---	---	---	---	---	---	---	---	---

MSB of instruction is ALWAYS the MSB of the immediate. Sign-extending is just copying the MSB, and almost all RISC-V immediates sign-extend. **To sign-extend, we just take the MSB of the instruction.**

[illegible]

Tracking all Immediate Bits in each format

Imm	31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
-----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	---	---	---	---	---	---	---	---	---	---

Bits 31-21 and 19-12 of immediate: Always the corresponding bit in the instruction if part of the format, and **bit 31** otherwise. **Only two options for these bits as well**

I	31	30	29	28	27	26	25	24	23	22	21	20																				
S	31	30	29	28	27	26	25															10	9	8	7	6	5	4	3	2	1	0
B	31	30	29	28	27	26	25															10	9	8	7	6	5					
U	31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12												
J	20	10	9	8	7	6	5	4	3	2	1	11	19	18	17	16	15	14	13	12												

Tracking all Immediate Bits in each format

CS 61C

Summer 2025

Imm	31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
-----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	---	---	---	---	---	---	---	---	---	---

Bits 20 and 11 of immediate: Kind of put in random spots where there's space. Bit 20 needs a 2-way mux, and bit 11 needs a 4-way mux

I	11	10	9	8	7	6	5	4	3	2	1	0																				
S	11	10	9	8	7	6	5															4	3	2	1	0						
B	12	10	9	8	7	6	5															4	3	2	1	11						
U	31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12												
J	20	10	9	8	7	6	5	4	3	2	1	11	19	18	17	16	15	14	13	12												


How to make the ImmGen

Because of how all instruction formats were chosen, there are a lot of underlying patterns in how immediates are stored.

By looking for these patterns, the ImmGen can be greatly simplified (in terms of total number of logic gates)

- 6-select 32-bit mux = 640 logic gates (counting 2-input OR and ANDs, and 1-input NOTs)
- Using just muxes for each set of bits, you can get this down to 160 logic gates (best Justin got)
 - Con: Makes it harder to extend your CPU. Often not worth it to optimize this too much
- Exact details left for Project 3B

Complete RISC-V Datapath!

 


Agenda

- Implementing Branches
- Implementing U-types
- Implementing ImmGen
- **Datapath and Control**
 - Control Logic Design: ROM
 - Control Logic Design: Combinational Logic
- Instruction Timing

Complete RISC-V Datapath

CS 61C

Summer 2025

 

[Practice] RV32I Datapath and Control


For each instruction below:

- a. Which wires should hold relevant data, i.e., what is the “lit up” datapath?
- b. What should the control signals be set to?
- c. Does this instruction use all 5 phases?

1. `add rd rs1 rs2`
2. `beq rs1 rs2 offset`
3. `sw rs2 imm(rs1)`
4. `lw rd imm(rs1)`

 1. add rd rs1 rs2
2. beq rs1 rs2 offset
3. sw rs2 imm(rs1)
4. lw rd imm(rs1)

- Which wires should hold relevant data?
- What should the control signals be set to?
- Does this instruction use all 5 phases?



1. `add rd rs1 rs2`
2. `beq rs1 rs2 offset`
3. `sw rs2 imm(rs1)`
4. `lw rd imm(rs1)`

- Which wires should hold relevant data?
- What should the control signals be set to?
- Does this instruction use all 5 phases?

Scratch Work:

Control Logic Truth Table (Partial)

Do Project 3!

inst[31:0]	BrEq	BrLT	PCSel	ImmSel	BrUn	ASel	BSel	ALUSel	MemRW	RegWEn	WBSel
R-Type	*	*	+4	*	*	Reg	Reg	(Op)	Read	1	ALU
add								Add			
sub								Sub			
addi	*	*	+4	I	*	Reg	Imm	Add	Read	1	ALU
lw	*	*	+4	I	*	Reg	Imm	Add	Read	1	Mem
sw	*	*	+4	S	*	Reg	Imm	Add	Write	0	*
beq				B	*	PC	Imm	Add	Read	0	*
not taken	0	*	+4								
taken	1	*	ALU								
bne				B	*	PC	Imm	Add	Read	0	*
taken	0	*	ALU								
not taken	1	*	+4								
blt taken	*	1	ALU	B	0	PC	Imm	Add	Read	0	*
bltu taken	*	1	ALU	B	1	PC	Imm	Add	Read	0	*
jalr	*	*	ALU	I	*	Reg	Imm	Add	Read	1	PC+4
jal	*	*	ALU	J	*	PC	Imm	Add	Read	1	PC+4
auipc	*	*	+4	U	*	PC	Imm	Add	Read	1	ALU

Agenda

- Implementing Branches
- Implementing U-types
- Implementing ImmGen
- Datapath and Control
 - **Control Logic Design: ROM**
 - Control Logic Design: Combinational Logic
- Instruction Timing

Two Options for Control Realization

1. Read-Only-Memory (ROM)

- a. Regular structure
- b. Can be easily reprogrammed to...
 - i. fix errors
 - ii. add instructions
- c. Popular when designing control logic manually

2. Combinational Logic

- a. Instead of ROM, design with gates (AND, OR, NOT)
- b. Popular for chip design (fast)
- c. Today, chip designers use logic synthesis tools to convert truth tables to networks of gates.


RV32I ROM-based Control

1. Read-Only-Memory (ROM) reads out a word at a given address.
2. To get control signals:
 - a. Input Address: Relevant set of instruction bits
 - b. Output word: Bits of control signals

1. What is the minimum set of instruction bits needed for input (RV32I)?

2. Why might PCSel not be known at this time?

 - A. 32
B. 17
C. 11
D. 9
E. Something else



RV32I is a “9-bit ISA”

CS 61C

1. `inst[30]`
 - a. `funct7`
 - b. `add/sub, sll/srl`
2. `inst[14:12]`
 - a. `funct3`
3. `inst[6:2]`
 - a. `opcode`
 - b. `inst[1:0]` fixed in RV32I, changes with extensions (e.g., compressed instructions)


Summer 2025

imm[31:12]				rd	0110111	LUI	
imm[31:12]				rd	0010111	AUIPC	
imm[20:10:11:19:12]				rd	1101111	JAL	
imm[11:0]		rs1	000	rd	1100111	JALR	
imm[12:10:5]	rs2	rs1	000	imm[4:1:11]	1100011	BEQ	
imm[12:10:5]	rs2	rs1	001	imm[4:1:11]	1100011	BNE	
imm[12:10:5]	rs2	rs1	100	imm[4:1:11]	1100011	BLT	
imm[12:10:5]	rs2	rs1	101	imm[4:1:11]	1100011	BGE	
imm[12:10:5]	rs2	rs1	110	imm[4:1:11]	1100011	BLTU	
imm[12:10:5]	rs2	rs1	111	imm[4:1:11]	1100011	BGEU	
imm[11:0]		rs1	000	rd	0000011	LB	
imm[11:0]		rs1	001	rd	0000011	LH	
imm[11:0]		rs1	010	rd	0000011	LW	
imm[11:0]		rs1	100	rd	0000011	LBU	
imm[11:0]		rs1	101	rd	0000011	LHU	
imm[11:5]		rs2	rs1	000	imm[4:0]	0100011	SB
imm[11:5]		rs2	rs1	001	imm[4:0]	0100011	SH
imm[11:5]		rs2	rs1	010	imm[4:0]	0100011	SW
imm[11:0]		rs1	000	rd	0010011	ADDI	
imm[11:0]		rs1	010	rd	0010011	SLTI	
imm[11:0]		rs1	011	rd	0010011	SLTIU	
imm[11:0]		rs1	100	rd	0010011	XORI	
imm[11:0]		rs1	110	rd	0010011	ORI	
imm[11:0]		rs1	111	rd	0010011	ANDI	
0000000		shamt	rs1	001	rd	0010011	SLLI
0000000		shamt	rs1	101	rd	0010011	SRLI
0100000		shamt	rs1	101	rd	0010011	SRAI
0000000		rs2	rs1	000	rd	0110011	ADD
0100000		rs2	rs1	000	rd	0110011	SUB
0000000		rs2	rs1	001	rd	0110011	SLL
0000000		rs2	rs1	010	rd	0110011	SLT
0000000		rs2	rs1	011	rd	0110011	SLTU
0000000		rs2	rs1	100	rd	0110011	XOR
0000000		rs2	rs1	101	rd	0110011	SRL
0100000		rs2	rs1	101	rd	0110011	SRA
0000000		rs2	rs1	110	rd	0110011	OR
0000000		rs2	rs1	111	rd	0110011	AND
fm	pred	succ	rs1	000	rd	0001111	FENCE
000000000000			00000	000	00000	1110011	ECALL
000000000001			00000	000	00000	1110011	EBREAK

RV32I ROM-based Control


PCSel cannot be encoded in our ROM because it depends on subsequent datapath output (branch comparator).

CS 61C

 

ROM Controller Implementation

 Under the hood, the ROM controller can be implemented as combinational logic gates. Use Sum of Products on logic table.



Agenda

- Implementing Branches
- Implementing U-types
- Implementing ImmGen
- Datapath and Control
 - Control Logic Design: ROM
 - **Control Logic Design: Combinational Logic**
- Instruction Timing

Combinational Logic-based Control Logic

- Much harder than ROM approach
 - We won't be able to help as much in OH
- But also lets you see the beauty of RISC-V's underlying design
- Goal: Build a combinational logic circuit that computes each individual control signal, using the 9 relevant bits of the opcode and funct3/funct7
- Compared to a ROM or comparator-based approach, uses significantly fewer gates (1000+ vs 25 gates)

[Practice] Combinational Logic-based Control Logic

- Write boolean expressions for:
 - BrUn
 - ASel
 - BSel
 - RegWEn
 - You can do more too!

[Practice] Write a Boolean Expression for BrUn

Instruction	Opcode	Funct3
beq rs1 rs2 label	110 0011	000
bne rs1 rs2 label	110 0011	001
blt rs1 rs2 label	110 0011	100
bltu rs1 rs2 label	<u>110</u> <u>0011</u>	<u>110</u>
bge rs1 rs2 label	110 0011	101
bgeu rs1 rs2 label	<u>110</u> <u>0011</u>	<u>111</u>

31	25	24	20	19	15	14	12	11	7	6	0
B	imm[12 10:5]			rs2		rs1		funct3	imm[4:1 11]		opcode

BrUn =

`!inst[2]&!inst[3]&!inst[4]&inst[5]&inst[6]&inst[13]`

[Practice] Write a Boolean Expression for BrUn

Instruction	Opcode	Funct3
beq rs1 rs2 label	110 0011	000
bne rs1 rs2 label	110 0011	001
blt rs1 rs2 label	110 0011	100
bltu rs1 rs2 label	<u>110 0011</u>	<u>110</u>
bge rs1 rs2 label	110 0011	101
bgeu rs1 rs2 label	<u>110 0011</u>	<u>111</u>

For non-Branch instructions, BrUn is *, not 0. So we don't actually need to check the opcode bits!

31	25	24	20	19	15	14	12	11	7	6	0
B	imm[12 10:5]	rs2	rs1	funct3	imm[4:1 11]	opcode					

BrUn = inst[13]

Combinational Logic-based Control Logic

- Much harder than ROM approach
 - We won't be able to help as much in OH
- But also lets you see the beauty of RISC-V's underlying design
- Goal: Build a combinational logic circuit that computes each individual control signal, using the 9 relevant bits of the opcode and funct3/funct7
- Compared to a ROM or comparator-based approach, uses significantly fewer gates (1000+ vs 25 gates)
- General approach: Find patterns in instructions, take advantage of * values to minimize circuit complexity. Handle each bit separately.

Agenda

- Implementing Branches
- Implementing U-types
- Implementing ImmGen
- Datapath and Control
 - Control Logic Design: ROM
 - Control Logic Design: Combinational Logic
- **Instruction Timing**


Instructions' Critical Path

For each of the below instructions, what is the delay along the critical path?


1. **add rd rs1 rs2**
2. **lw rd imm(rs1)**

 - A. $t_{clk_q} + t_{Add} + t_{MEM} + t_{Reg} + t_{BrComp} + t_{ALU} + t_{DMEM} + t_{mux} + t_{Setup}$
- B. $t_{clk_q} + t_{MEM} + t_{Reg} + t_{mux} + t_{ALU} + t_{mux} + t_{setup}$
- C. $t_{clk_q} + t_{MEM} + \max\{t_{Reg}, t_{lmm}\} + t_{ALU} + 2*t_{mux} + t_{DMEM} + t_{Setup}$
- D. $t_{clk_q} + t_{MEM} + \max\{t_{Reg}, t_{lmm}\} + t_{ALU} + 3*t_{mux} + t_{Setup}$
- E. Something else

Critical Path for Add: $t_{clk_q} + t_{IMEM} + t_{Reg} + t_{mux} + t_{ALU} + t_{mux} + t_{setup}$




 Critical Path for lw: $t_{clk_q} + t_{IMEM} + \max\{t_{Reg}, t_{Imm}\} + t_{ALU} + 2 \cdot t_{mux} + t_{DMEM} + t_{Setup}$



Instruction Timing, Divided by 5 Phases

 - To estimate maximum clock frequency, analyze at a higher level.
- Assume each phase is **dominated** by major functional HW units:




Compute Clock Period

- The clock cycle must encompass the **longest critical path delay** incurred by any instruction.

Instruction	IF (200ps)	ID (100ps)	EX (200ps)	MEM (200ps)	WB (100ps)	Total
add	X	X	X		X	600ps
beq	X	X	X			500ps
jal	X	X	X			500ps
<u>lw</u>	X	X	X	X	X	800ps
sw	X	X	X	X		700ps

- Maximum Clock Frequency:
 - $f_{\max} = 1/800 \text{ ps} = 1.25 \text{ GHz}$
 - However, not all instructions use all HW blocks.
- Many blocks are idle most of the time...!
 - Conversely, each phase just takes 200 ps $\rightarrow$ could clock 5GHz...??

5-Phase Timing, In Detail

 

Agenda

- Implementing Branches
- Implementing U-types
- Implementing ImmGen
- Datapath and Control
 - Control Logic Design: ROM
 - Control Logic Design: Combinational Logic
- Instruction Timing
- **And in Conclusion**

Call home, we've made HW/SW contact!

High Level Language
Program (e.g., C)

Compiler

Assembly Language
Program (e.g., RISC-V)

Assembler

Machine Language Program
(RISC-V)

Hardware Architecture Description
(e.g., block diagrams)


Architecture Implementation

Logic Circuit Description
(Circuit Schematic Diagrams)

```
temp = v[k];  
v[k] = v[k+1];  
v[k+1] = temp;
```

```
lw    x3, 0(x10)  
lw    x4, 4(x10)  
sw    x4, 0(x10)  
sw    x3, 4(x10)
```
 
```
1000 1101 1110 0010  
1000 1110 0001 0000  
1010 1110 0001 0010  
1010 1101 1110 0010
```



“And in conclusion...”

- We have built a processor!
 - Capable of executing all RISC-V instructions in one cycle each
- Not all HW units used by all instructions
 - The **critical path changes** based on instruction.
- 5 Phases of execution
 - IF, ID, EX, MEM, WB
 - Not all instructions are active in all phases
- Controller specifies how to execute instructions
 - Implemented as ROM or logic
- Next:
 - Making our single-stage CPU faster